

P441/P442 - Open Lab Experiment

# NON-LINEAR DYNAMICS CIRCUIT

*Submitted By*

**ASHMITA PANDA**

**ROLL NO. 1811042**

School of Physical Sciences

National Institute of Science, Education and Research (NISER), Bhubaneswar

Date of Submission : 24<sup>th</sup> September, 2021

*Under the Guidance of*

**Dr. Pratap Kumar Sahoo**

Associate Professor

School of Physical Sciences

National Institute of Science Education and Research (NISER), Bhubaneswar



# Contents

	Page
<b>1. Introduction</b>	<b>1</b>
<b>2. Theoretical Design</b>	<b>1</b>
2.1 Circuit Elements and Constraints	1
2.2 Possible Configurations	2
2.3 Final Circuit	3
<b>3. State Equations and Simulations</b>	<b>4</b>
3.1 State Equations	4
3.2 Simulation	4
3.2.1 Python Codes	5
3.2.2 Plots with Dimensionless Constants	6
3.2.3 Varying R with Dimensionful Constants	8
3.3 Problems with Simulation	13
<b>4. Simulation to Practical Design</b>	<b>13</b>
4.1 Negative Resistance	13
4.1.1 Voltage Controlled Voltage Source	13
4.1.2 Negative Resistance using ideal VCVS	14
4.1.3 Op-Amps as VCVS	16
4.1.4 Negative Resistance using Op-Amps	17
4.2 Non-Linear Resistance	20
<b>5. Practical Implementation with LTSpice</b>	<b>22</b>
5.1 Setting Component Values	22
5.2 Negative Resistances	23
5.2.1 $N_{R1}$	23

# Abstract

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Etiam lobortis facilisis sem. Nullam nec mi et neque pharetra sollicitudin. Praesent imperdiet mi nec ante. Donec ullamcorper, felis non sodales commodo, lectus velit ultrices augue, a dignissim nibh lectus placerat pede. Vivamus nunc nunc, molestie ut, ultricies vel, semper in, velit. Ut porttitor. Praesent in sapien. Lorem ipsum dolor sit amet, consectetur adipiscing elit. Duis fringilla tristique neque. Sed interdum libero ut metus. Pellentesque placerat. Nam rutrum augue a leo. Morbi sed elit sit amet ante lobortis sollicitudin. Praesent blandit blandit mauris. Praesent lectus tellus, aliquet aliquam, luctus a, egestas a, turpis. Mauris lacinia lorem sit amet ipsum. Nunc quis urna dictum turpis accumsan semper.

---

## I. Introduction

Chua circuit is the simplest electronic circuit which exhibits the phenomenon of chaos. It was invented by Leon Chua in 1983.

A dynamical system is said to have chaotic behaviour when despite its deterministic nature, it is not predictable. The apparent random behaviour of the system is usually governed by deterministic laws that are highly sensitive to initial conditions. A small change in initial conditions can result in widely varying results.

To exhibit chaos, a circuit must have been :

- i.) at least one locally active resistor
- ii.) at least one non-linear element
- iii.) at least three energy storage units

## II. Theoretical Design

### 2.1 Circuit Elements and Constraints

In order to physically exhibit the phenomenon of chaos Chua decided to design a physical circuit with 3 unstable equilibrium points with further constraints that number of passive elements should be as few as possible and there should be only one non-linear resistor with

two terminals which has piecewise linear characteristic.

There must be 3 energy storage elements as the dynamical system must have at least order 3 to be chaotic. He also decided to have only one passive element in the circuit - a linear resistor.

Passive elements are the circuit elements which donot generate power but instead store or dissipate it.

Also since we want to observe oscillations, we cannot have only capacitors or only inductors as all 3 energy storage elements. There must be some combination of both. Chua preferred the combination of two capacitors and one inductor to make the circuit more cost-efficient.

## 2.2 Possible Configurations

With these constraints in place, there can be 8 possible configurations.

Fig 1. Possible configurations for the circuit


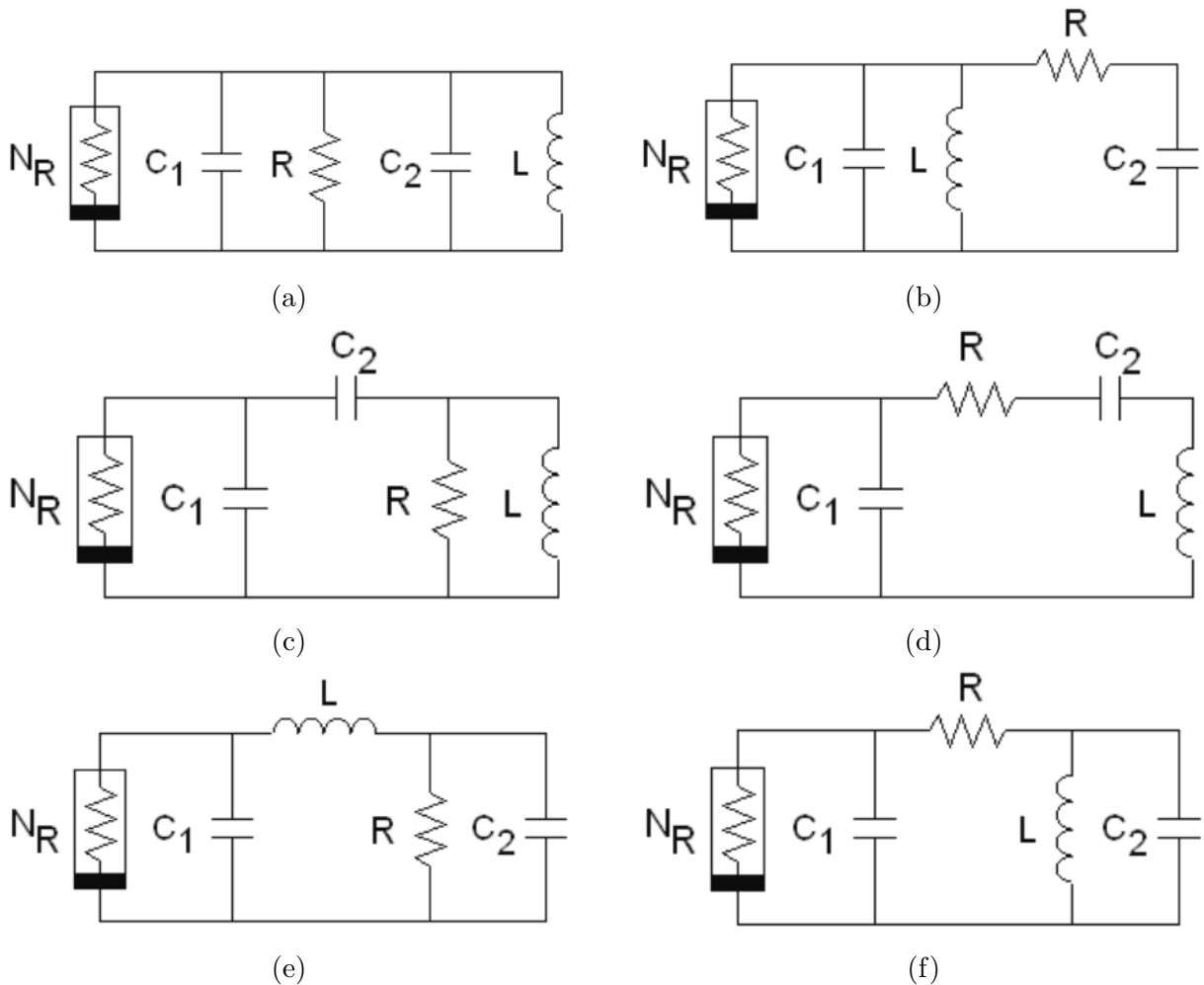


Fig 1. Possible configurations for circuit

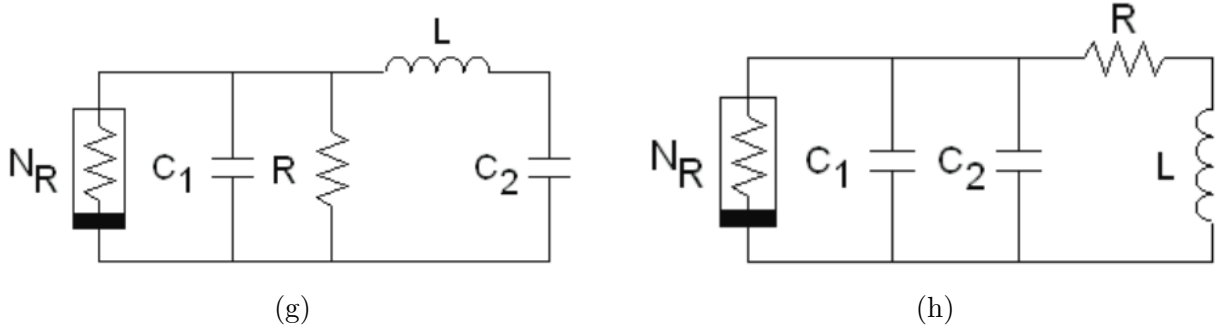

Configuration (g) and (h) can be immediately rejected.

In (g) the characteristic of resistance  $R$  can be absorbed in the characteristics of non-linear resistor  $N_R$ . In (h) the  $C_1$  and  $C_2$  capacitances can be replaced by a single effective capacitor  $C = C_1 + C_2$ . So in both of these configurations all circuit elements donot give unique contribution. Thus they can be rejected.

For (a) and (b), the DC equilibrium calculations show that non-linear resistor gets short-circuited by the inductor. For (c) and (d), the DC equilibrium calculations show that non-linear resistor terminals are open. So all the four configurations can be rejected.

The remaining configuration (e) and (f) are both valid, but Chua selected configuration (f) because the RLC subcircuit generates oscillations.

## 2.3 Final Circuit

The final Chua circuit is given as follows :

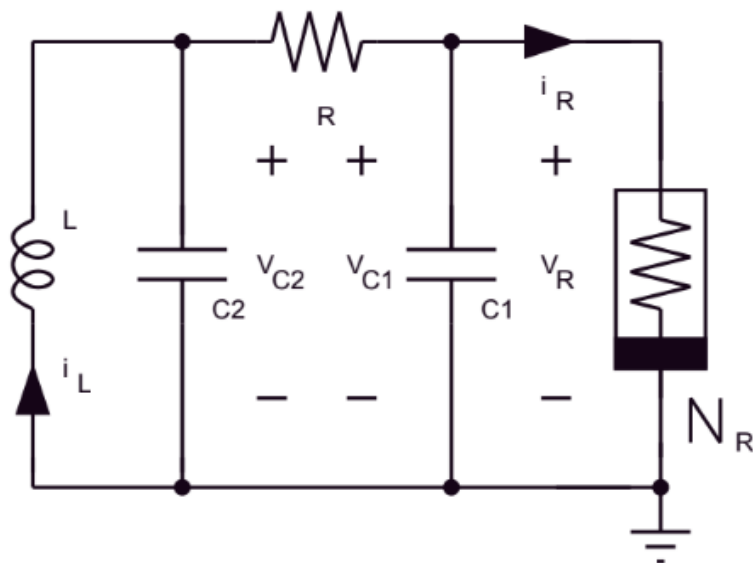


Fig 2. Chua's Circuit

# III. State Equations and Simulations

## 3.1 State Equations

The equations of Chua's circuit are given as a system of three coupled differential equations :

$$C_1 \frac{dv_{C_1}}{dt} = G (v_{C_2} - v_{C_1}) - g(v_{C_1}) \quad (1)$$

$$C_2 \frac{dv_{C_2}}{dt} = G (v_{C_1} - v_{C_2}) - i_L \quad (2)$$

$$L \frac{di_L}{dt} = -v_{C_2} \quad (3)$$

where,  $G = \frac{1}{R}$  is the conductance, and  $g(x)$  is a piece-wise linear function. It is given as :

$$g(v) = m_0 v + \frac{1}{2}(m_1 - m_0) [|v + B_p| - |v - B_p|] \quad (4)$$

where,

$m_0 \implies$  slope of outer region

$m_1 \implies$  slope of inner region

$B_p \implies$  breakpoints (both positive and negative values)

## 3.2 Simulation

The variables were redefined and all constants were taken to right hand side to make handling the equations easier.

$$\frac{dx}{dt} = \frac{1}{C_1} \{G (y - x) - g(x)\} \quad (5)$$

$$\frac{dy}{dt} = \frac{1}{C_2} \{G (x - y) - z\} \quad (6)$$

$$\frac{dz}{dt} = -\frac{y}{L} \quad (7)$$

where,

$$x \equiv v_{C_1} \quad y \equiv v_{C_2} \quad z \equiv i_L$$

The equation  $g(x)$  remains the same as in (4).

The equations are solved numerically using Runge Kutta 4 method in Python. All plots are made using Gnuplot.

### 3.2.1 Python Codes

The code for RK4 is as follows :

```
1 #Chua circuit simulations
2
3 import math
4 import handling_files
5 import numpy as np
6
7 #RK4 to solve Chua circuit equations (a system of 3-ODEs)
8 def RK4_chua(F,b,t,h,N,name):
9     handling_files.append_file(name, f'{t} {b[0]} {b[1]} {b[2]}\n')
10    for i in range(N):
11        K1=F(t,b)
12        #
13        K2=F(t+h/2, b+np.multiply(K1,h/2))
14        #
15        K3=F(t+h/2, b+np.multiply(K2,h/2))
16        #
17        K4=F(t+h, b+np.multiply(K3,h))
18        #
19        b=b+np.multiply((K1+np.multiply(K2,2)+np.multiply(K3,2)+K4), h/6)
20        t=t+h
21        handling_files.append_file(name, f'{t} {b[0]} {b[1]} {b[2]}\n')
22        #
23    return(1)
```

The code inputs the three differential equations as a column vector  $F$  which is a function of  $x$ ,  $y$ ,  $z$  and  $t$  (time).  $x$ ,  $y$  and  $z$  are arranged as column vector  $b$ . For the first iterations, it has the initial values.  $h$  is the increment factor.  $N$  is the number of iterations.  $t_0$  is the initial time value.

The 'append.file()' function saves the data points ( $t$ ,  $x$ ,  $y$  and  $z$ ) after each iteration in a file (filename provided to function as variable 'name'). All codes for manipulation with files is as follows :

```
1 #Library for handling files and their contents
2
3 # READ FILE
4 def read_matrix(x): #more than one column #parameter = name of file
5     f=open(x,'r') # 'r' ==> read only
6     X=[[float(num) for num in line.split('\t')] for line in f]
7     f.close()
8     return(X)
9
10 #
11 #####
```

```

11
12 # APPEND FILE
13 def append_file(x, str): #arguments = name of file, string to append
14     f=open(x, 'a') #'a' ==> append file
15     f.write(str)
16     f.close()
17     #
18
19 #
20 #####
21
22 #WRITE AT BEGINNING (hopefully)
23 def write_beginning(x, str):
24     f=open(x, 'r+')
25     old=f.read()
26     f.seek(0)
27     f.write(str + old)
28     f.close()
29     # it works :D
30
31 # PRINT CONTENTS OF A TEXT FILE
32 def print_file(x): #argument = name of file
33     f=open(x, 'r')
34     contents=f.read()
35     print(contents)
36
37 #
38 #####

```

### 3.2.2 Plots with Dimensionless Constants

The following values were used for the constants :

$$G = 0.7 \quad C_1 = 1/9 \quad C_2 = 1 \quad L = 1/7 \quad B_p = 1 \quad m_0 = -0.5 \quad m_1 = -0.8$$

The function  $g(v)$  in (4) can be plotted using the constants.



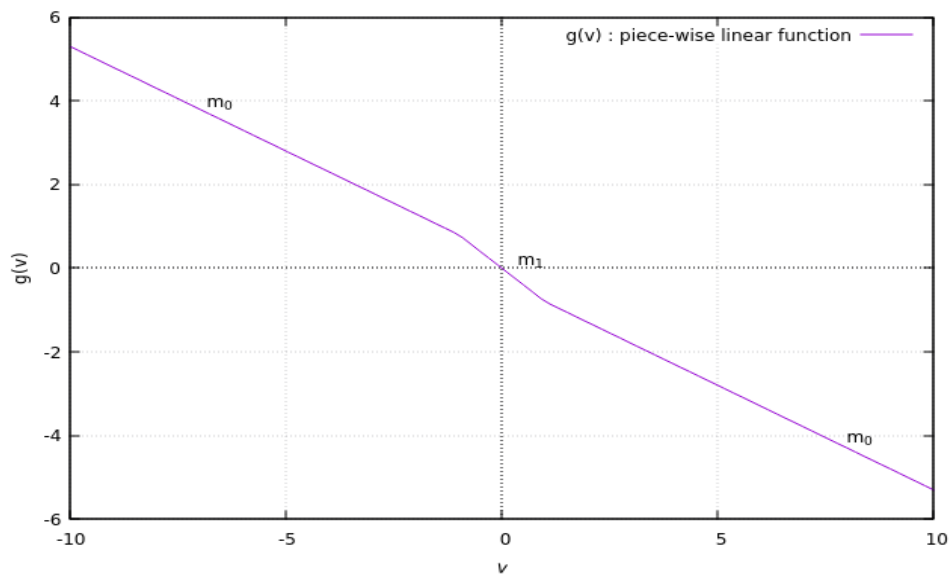


Fig 3. Three Segment Linear Function :  $g(v)$

The code for defining the function, initial values and calling the function is :

```

1 # Dimensionless Chua Circuit
2
3 import math
4 import sys
5 import numpy as np
6
7 sys.path.append('/home/ashmita/Desktop/ASHMITA/APanda_Lib')
8 # importing all files at once, now we just need to write function name to
   access it
9 from APanda_Lib import *
10
11 import chua_circuit_simulations
12
13 #dimensionless chua
14 R=1.4285 # R corresponding to G=0.7
15 C1=1/9
16 C2=1
17 L=1/7
18 Bp=1
19 m0=-0.5
20 m1=-0.8
21
22 x0=0.1
23 y0=0.0
24 z0=0.0
25 t0=0.0
26
27 b0=[x0, y0, z0]
28
29 def Yfunc(t,b):

```

```

30     x,y,z=b
31     gx=m0*x+0.5*(m1-m0)*(abs(x+1)-abs(x-1))
32     Y=[(1/C1)*((1/R)*(y-x)-gx), (1/C2)*((1/R)*(x-y)+z), (-1/L)*y]
33     return Y
34     #
35
36 h=0.1
37 N=5000
38 path="/home/ashmita/Desktop/ASHMITA/NISER Study/7th Semester/Open Lab/Non-
    Linear Circuit/Dimensionless/"
39 name=f'dimensionless'
40 n=path+name
41 f=open(n, "w")
42 f.close()
43 out2=chua_circuit_simulations.RK4_chua(Yfunc,b0,t0,h,N,n)
44 #

```

The data file obtained is plotted using Gnuplot.

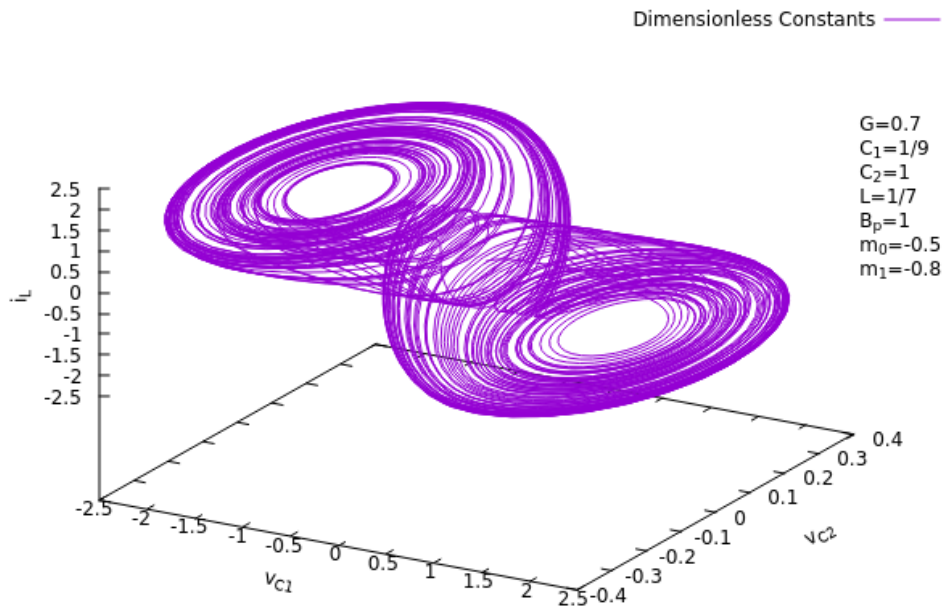


Fig 4. 3D plot of  $v_{C1}$  vs  $v_{C2}$  for dimensionless constants

Thus, we do obtain a double scroll attractor for the Chua Circuit. In principle, the Chua Circuit does exhibit chaotic behaviour.

### 3.2.3 Varying $R$ with Dimensionful Constants

Now, we will attempt to use constants which represent actual dimensionful values and try to observe how the graph changes when we change the value of resistance  $R$ .

We will define conversion factors to relate the value of our constants to values of actual electronic circuit components. Current will be measured in Amperes(A), potential differences in Volts(V), capacitances in Farads(F), inductance in Henry(H) and resistance in Ohm( $\Omega$ ). Resistivity is expressed in Siemens(S)

If we want currents of milliamperes to be in the circuit, we will adjust all current values by 1000. It will thus increase resistances and inductance by 1000, while decreasing capacitances by the same factor. Also, we can also rescale the values of time by some factor k in (3). This will leave all resistances unaffected, and all capacitors and inductors will be scaled by same factor k. For ease of using values in the code, I have chosen k to be  $10^{-4}$ , i.e., I rescale all capacitances and inductances by  $10^{-4}$ . This gives us the final conversion factors as :

$$\begin{aligned} R : 1 &\equiv 1000\Omega = 1k\Omega \\ C_1, C_2 : 1 &\equiv 10^{-7}F = 100nF \\ L : 1 &\equiv 10^{-1}H = 100mH \\ m_0, m_1 : 1 &\equiv 10^{-3}S = 1mS \\ B_p : 1 &\equiv 1V \end{aligned}$$

So, the constants used in the previous part correspond to :

$$R = 1.43k\Omega ; C_1 = 11.11nF ; C_2 = 100nF ; L = 14.29mH ; B_p = 1V ; m_0 = -0.5mS ; m_1 = -0.8mS$$

We will now attempt to vary R and observe how the output changes.

The code for defining the function, initial values, varying R values and calling the function is :

```

1 # Varying R
2
3 import math
4 import sys
5 import numpy as np
6
7 sys.path.append('/home/ashmita/Desktop/ASHMITA/APanda_Lib')# importing all
   files at once
8 from APanda_Lib import *
9
10 import chua_circuit_simulations
11
12 #varying R
13 R=float(input('Please enter the value of R.\n'))
14 C1=1/9
15 C2=1
16 L=1/7
17 Bp=1
18 m0=-0.5

```


```

19 m1=-0.8
20
21 x0=0.1
22 y0=0.0
23 z0=0.0
24 t0=0.0
25
26 b0=[x0, y0, z0]
27
28 def Yfunc(t,b):
29     x,y,z=b
30     gx=m0*x+0.5*(m1-m0)*(abs(x+1)-abs(x-1))
31     Y=[(1/C1)*((1/R)*(y-x)-gx), (1/C2)*((1/R)*(x-y)+z), (-1/L)*y]
32     return Y
33     #
34
35 h=0.1
36 N=5000
37 path="/home/ashmita/Desktop/ASHMITA/NISER Study/7th Semester/Open Lab/Non-
    Linear Circuit/Varying R/"
38 name=f'R={R}'
39 n=path+name
40 f=open(n, "w")
41 f.close()
42 out2=chua_circuit_simulations.RK4_chua(Yfunc,b0,t0,h,N,n)
43 #


```

Plotting the data files obtained in Gnuplot.


Fig 5. R Bifurcation in Theoretical Chua Circuit using a Three Segment Non-Linear Resistance

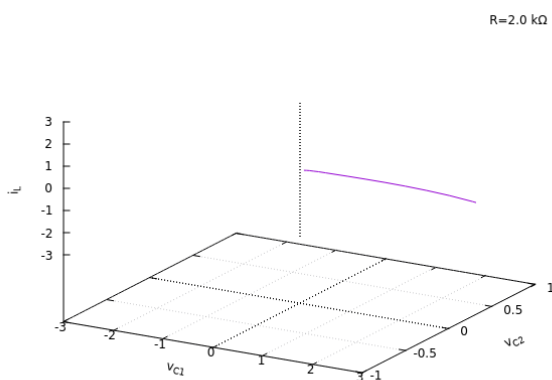


(a)  $R = 2.0k\Omega$

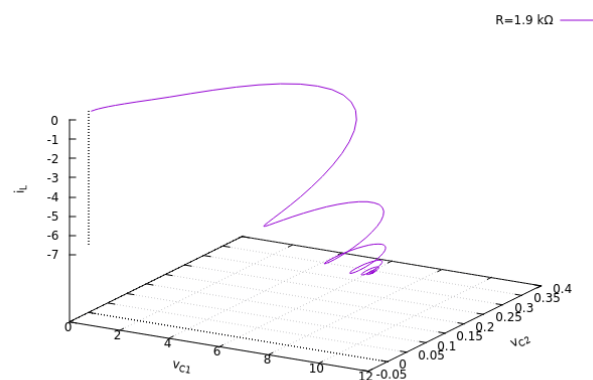


(b)  $R = 1.9k\Omega$

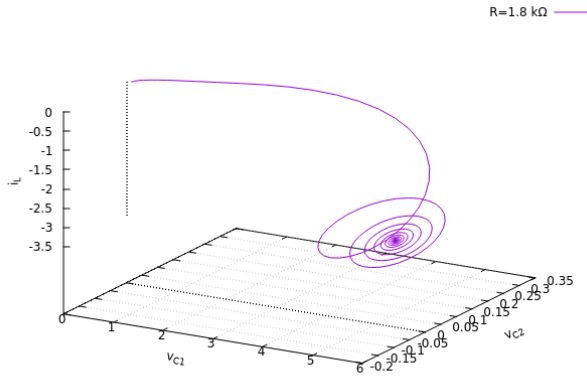


(c)  $R = 1.8k\Omega$

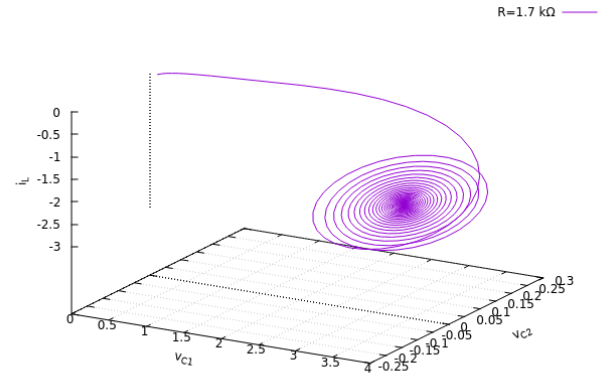


(d)  $R = 1.7k\Omega$

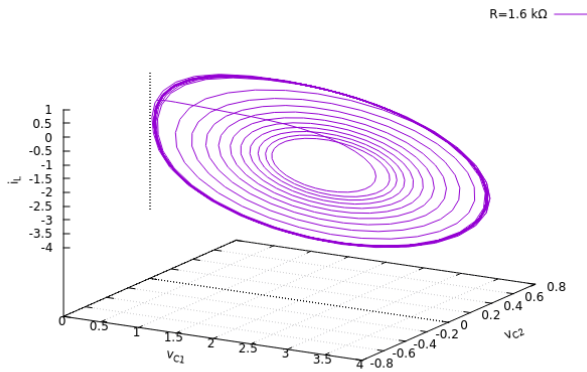


(e)  $R = 1.6k\Omega$

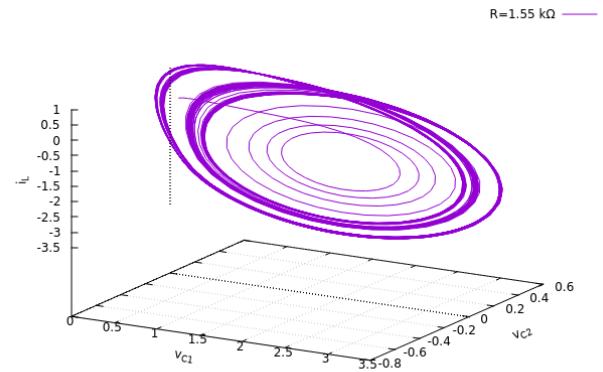


(f)  $R = 1.55k\Omega$

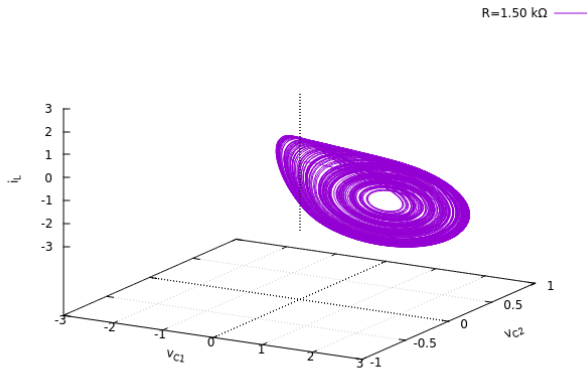


(g)  $R = 1.5k\Omega$

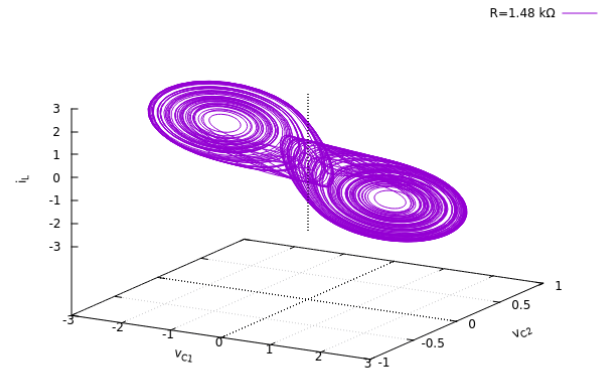


(h)  $R = 1.48k\Omega$

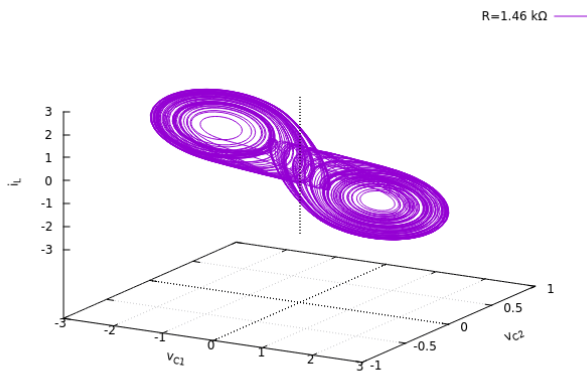


(i)  $R = 1.46k\Omega$

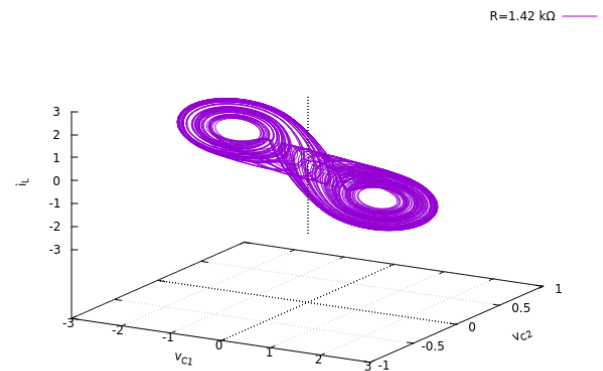


(j)  $R = 1.42k\Omega$

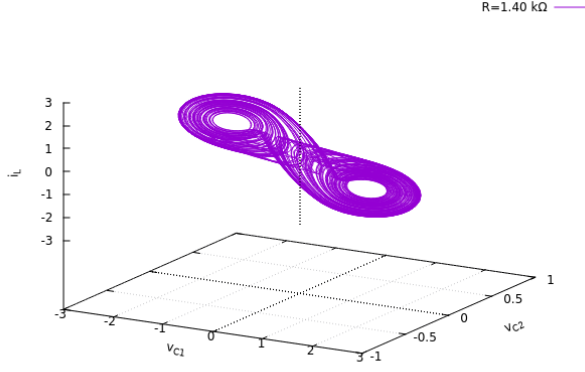


(k)  $R = 1.4k\Omega$

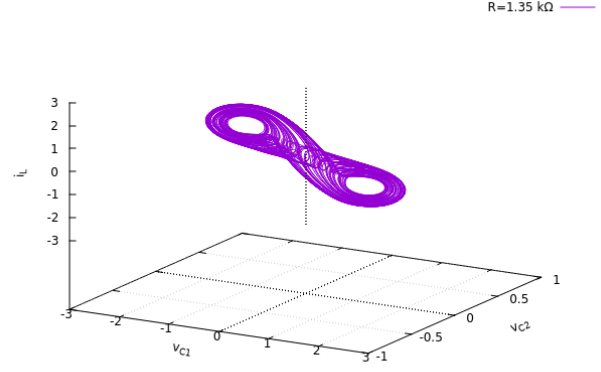


(l)  $R = 1.35k\Omega$

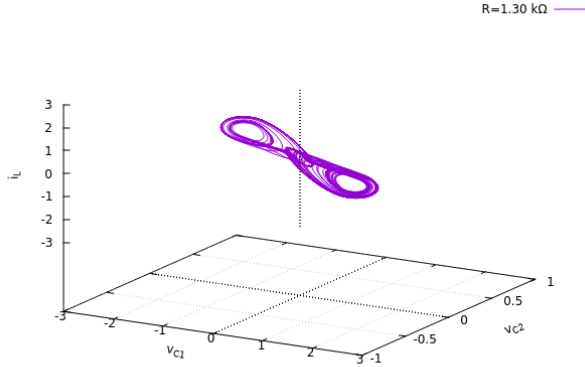


(m)  $R = 1.3k\Omega$

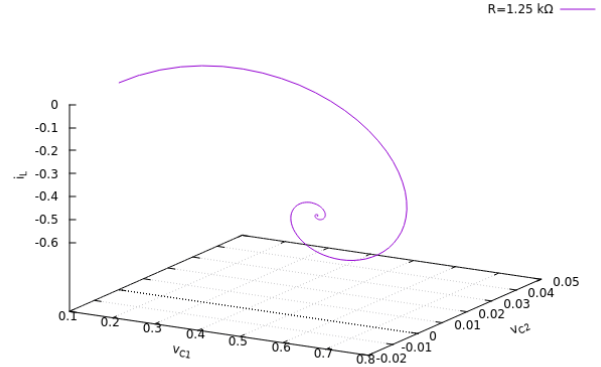

(n)  $R = 1.25k\Omega$

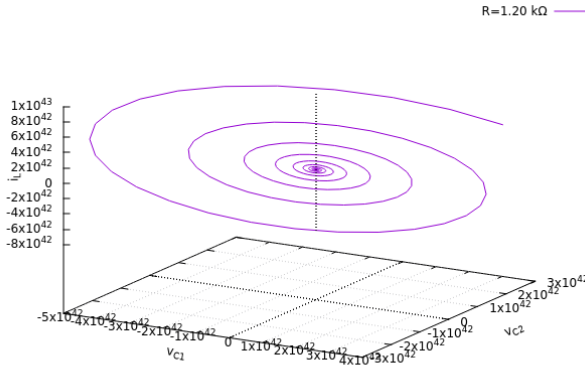

(o)  $R = 1.2k\Omega$

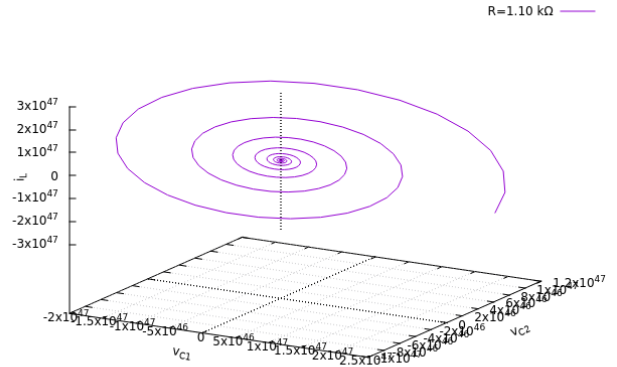

(p)  $R = 1.1k\Omega$

We observe that  $R = 2.0k\Omega$  shows DC Equilibrium. As resistance is reduced, the characteristics look like an unbounded spiral.

The Rossler Attractor forms around  $R = 1.5k\Omega$  and the Double Scroll Attractor is first formed at  $R = 1.48k\Omega$ . As the resistance is further reduced, the size of the double scroll also decreases.

By  $R = 1.25k\Omega$  the double scroll character is lost, and for lower resistances the graphs show a spiral with no upper bound. The values of  $v_{C1}$ ,  $v_{C2}$  and  $i_L$  apparently take values in the ranges of  $10^{43}$  and  $10^{47}$ . This is not physically possible.

### 3.3 Problems with Simulation

The current simulation of the Chua Circuit is not physically viable, as is evident from the graphs obtained for various values of resistance. It predicts that except for a small window of resistance values (from  $R = 1.5k\Omega$  to  $R = 1.3k\Omega$ ) the values of voltages and current is not bounded.

The problems arises because we have failed to take into account the fact that all physical resistors are eventually passive, i.e., for large enough values of voltages applied across its terminals, the power consumed by the resistor becomes positive.

In our current equation (4) and graph of  $g(v)$ , we see that the condition of eventual passivity has not been taken into account. The power consumed by the resistor is negative for all values of voltages.

## IV. Simulation to Practical Design

### 4.1 Negative Resistance

To implement a Chua Circuit practically we first need to construct a negative resistance which follows the characteristics of  $g(v)$  graph. One way to construct a negative resistance is to connect three positive linear resistors to a voltage controlled voltage source (VCVS).

#### 4.1.1 Voltage Controlled Voltage Source

A VCVS is defined to be an ideal circuit element with two input and two output terminals such that no current flows between the input terminals and voltage across output terminals is dependent on the voltage across input terminals.

$$v_o = f(v_d)$$

$f(\cdot)$  could have any functional dependence, but the simplest non-trivial relation occurs when it is linear.

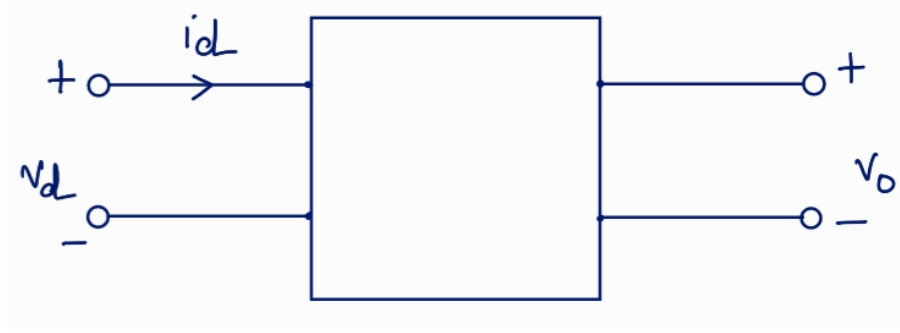


Fig 6. Voltage Controlled Voltage Source

#### 4.1.2 Negative Resistance using ideal VCVS

The circuit diagram to build a negative resistance using an ideal VCVS and three linear resistors is given as follows :

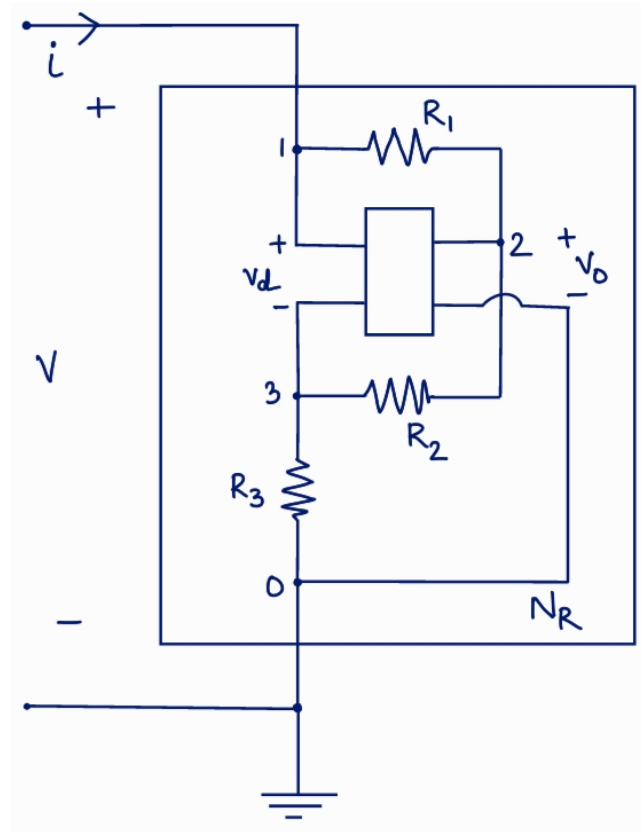


Fig 7. Negative Resistance using VCVS

Let us assume the VCVS follows a linear relationship :

$$v_o = Av_d \quad (8)$$

A is some proportionality constant.



Now, Kirchoff's Current Law (KCL) says that *for any node in an electrical circuit, the sum of the currents entering the node is equal to the sum of the currents leaving the node.*

Applying KCL on node (1) (in Fig 7):

$$i = i_1 \quad ; \quad i_1 = \frac{v - v_o}{R_1} \quad (9)$$

We can write this because no current goes inside VCVS.

Now, Kirchoff's Voltage Law (KVL) says that *if we move around a closed loop in a fixed direction then the sum of all the potential differences around the loop is zero.*

Applying KVL along loop 1-2-3-0 (in Fig 7):

$$v = v_d + i_3 R_3 \quad (10)$$

$$i_3 = \frac{v_o}{R_2 + R_3} \quad (11)$$

Using (11) in (10) :

$$v = v_d + \frac{v R_3 v_d}{R_2 + R_3} = \frac{R_2 + (1 + A) R_3}{R_2 + R_3} v_d$$

Now, using (8) in the above equation :

$$\therefore v = \left\{ \frac{R_2 + (1 + A) R_3}{A(R_2 + R_3)} \right\} v_o \quad (12)$$

We can now calculate the current  $i$  using (9) :

$$i = \frac{v}{R_1} - \frac{v_o}{R_1}$$

Using equation of  $v$  and  $v_o$  (12) :

$$\begin{aligned} \Rightarrow i &= \frac{v}{R_1} - \frac{1}{R_1} \left\{ \frac{A(R_2 + R_3)}{R_2 + (1 + A) R_3} v \right\} \\ \Rightarrow i &= \frac{v R_2 + v R_3 + v A R_3 - A R_2 v - A R_3 v}{R_1 [R_2 + (1 + A) R_3]} \end{aligned}$$

So we finally obtain :

$$\therefore i = \left\{ \frac{R_2(1 - A) + R_3}{R_1 [R_2 + (1 + A) R_3]} \right\} \quad (13)$$

Now if we take  $A$  to be very large,  $A \gg 1$ , greater than  $R_1, R_2$  and  $R_3$ , we can write :

$$\Rightarrow i \approx \frac{-R_2 A + R_3}{R_1(R_2 + R_3 A)} v$$

Also, as  $R_2 A \gg R_3$  and  $R_1 R_3 A \gg R_1 R_2$  :

$$\Rightarrow i \approx -\frac{R_2 A}{R_1 R_3 A} v \approx -\frac{R_2}{R_1 R_3} v$$

We can now set  $R_1 = R_2$ , and we obtain :

$$i = -\frac{1}{R_3} v \quad (14)$$

Thus it now appears that the segment  $N_R$  (in Fig 7) now has negative resistance  $-R_3$ .

### 4.1.3 Op-Amps as VCVS

An opamp is the practical or real-life approximation of a VCVS. The voltage applied across inverting and non-inverting terminals produces voltage at output terminal, if we take the reference terminal to be ground.

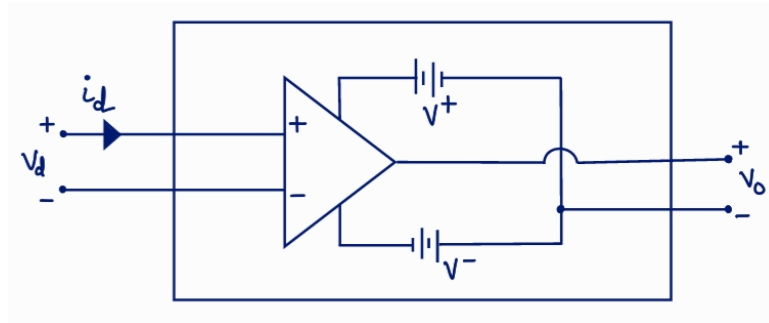


Fig 8. Op-amp as VCVS

Ideal opamps there is no current entering the circuit, i.e.,  $i_d = 0$  and the loop gain is infinite. But typically, most opamps produce output voltages 100,000 times larger than the potential difference between input terminals.

The output of a opamp becomes constant at some values of  $v_d = \pm E_{sat}$ .

$$\text{For } v_d \geq \frac{E_{sat}}{A} + v_{OS} : \text{ positive saturation region}$$

$$\text{For } v_d \leq -\frac{E_{sat}}{A} + v_{OS} : \text{ negative saturation region}$$

$$\text{For } -\frac{E_{sat}}{A} + v_{OS} < v_d < \frac{E_{sat}}{A} + v_{OS} : \text{ linear region}$$

$v_{OS}$  is the offset voltage.



From previous circuit analysis we have :

$$i = \frac{v - v_o}{R_1} \quad ; \quad v = v_d + \frac{R_3}{R_2 + R_3} v_o \quad ; \quad v_o = A v_d \quad (15)$$

As now we have an op-amp, there are three distinct regions depending on the voltage behavior :

$$\begin{aligned} \text{Negative Saturation :} \quad & v_o = -E_{sat} \quad ; \quad v_d \leq -\frac{E_{sat}}{A} \\ \text{Linear Region :} \quad & v_o = A v_d \quad ; \quad -\frac{E_{sat}}{A} < v_d < \frac{E_{sat}}{A} \\ \text{Positive Saturation :} \quad & v_o = E_{sat} \quad ; \quad v_d \geq \frac{E_{sat}}{A} \end{aligned}$$

### Positive Saturation

In the positive saturation region the output voltage is fixed at  $E_{sat}$ , even if the input changes.

$$v_o = E_{sat} \quad ; \quad v_d \geq \frac{E_{sat}}{A} \quad (16)$$

From (15) and (16), we have equation of current as :

$$i = \frac{v}{R_1} - \frac{E_{sat}}{R_1} \quad (17)$$

We can write the equation for voltage as :

$$\begin{aligned} v &= v_d + \frac{R_3}{R_2 + R_3} v_o \\ \Rightarrow v &\geq \frac{E_{sat}}{A} + \frac{R_3}{R_2 + R_3} E_{sat} \\ \Rightarrow v &\geq E_{sat} \left\{ \frac{R_2 + R_3 + A R_3}{A(R_2 + R_3)} \right\} \end{aligned}$$

So we finally obtain :

$$v \geq \left\{ \frac{R_2 + (1 + A)R_3}{A(R_2 + R_3)} \right\} E_{sat} \quad (18)$$

So the minimum value of valid  $v$  for positive saturation, or the positive breakpoint is given as :

$$B_P^+ = \frac{R_2 + (1 + A)R_3}{A(R_2 + R_3)} E_{sat} \quad (19)$$

Now if  $A$  is very large, we have  $(1 + A)R_3 + R_2 \rightarrow A R_3$ . So we obtain the breakpoint as :

$$B_P^+ \simeq \frac{R_3}{R_2 + R_3} E_{sat} \quad (20)$$

Slope of the graph is given as :

$$m_o = \frac{1}{R_1} \quad (21)$$

### Negative Saturation

In negative saturation,  $v_o = -E_{sat}$ . As all other equations remain same, we have the breakpoint as :

$$B_P^- = -\frac{R_2 + (1 + A)R_3}{A(R_2 + R_3)}E_{sat} \quad (22)$$

For very large A, we get the breakpoint as :

$$B_P^- \simeq -\frac{R_3}{R_2 + R_3}E_{sat} \quad (23)$$

The slope is still  $m_o$ .

### Linear Region

In the linear region, we have the standard circuit analysis we did before given in (15).

Writing voltage  $v_d$  in terms of  $v$  :

$$\begin{aligned} v &= v_d + \frac{R_3}{R_2 + R_3}v_o \\ \Rightarrow v &= v_d + \frac{R_3}{R_2 + R_3}Av_d \\ \Rightarrow v &= \frac{R_2 + (1 + A)}{R_2 + R_3}v_d \end{aligned}$$

Therefore, we obtain :

$$v_d = \frac{R_2 + R_3}{R_2 + (1 + A)R_3}v \quad (24)$$

Using this (24) to find current  $i$  :

$$i = \frac{(1 - A)R_2 + R_3}{R_1 [R_2 + (1 + A)R_3]}v \quad (25)$$

For large A, we have :

$$i \simeq -\frac{R_2}{R_1 R_3}v \quad (26)$$

The linear region is characterised by :

$$\begin{aligned} -\frac{E_{sat}}{A} &< v_d < \frac{E_{sat}}{A} \\ \Rightarrow -\frac{E_{sat}}{A} &< \frac{R_2 + R_3}{R_2 + (1 + A)R_3}v < \frac{E_{sat}}{A} \end{aligned}$$

For  $v$  :

$$\therefore -E_{sat} \frac{R_2 + (1 + A)R_3}{A(R_2 + R_3)} < v < E_{sat} \frac{R_2 + (1 + A)R_3}{A(R_2 + R_3)}$$

For large A, we have :

$$\Rightarrow -E_{sat} \frac{R_3}{R_2 + R_3} < v < E_{sat} \frac{R_3}{R_2 + R_3}$$

From (20) and (23) :

$$\therefore B_P^- < v < B_P^+$$

Thus, when voltage  $v$  lies between breakpoints, the op-amp functions in the linear region. Slope of the I-V graph in this region is :

$$m_1 = -\frac{R_2}{R_1 R_3} \quad (27)$$

The I-V characteristics of negative resistance implemented using op-amps should be of the form :

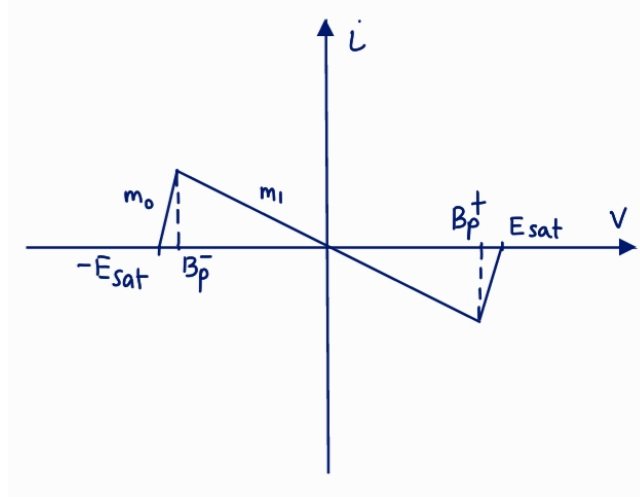


Fig 11. Expected I-V Characteristics of Negative Resistance

## 4.2 Non-Linear Resistance

Now that we have the negative resistances, we would like to implement our Non-Linear resistance to be used in the circuit. To do so, we need to put two negative resistances in parallel.

$N_{R_1}$  includes resistances  $R_1$ ,  $R_2$  and  $R_3$ . It has slopes  $m_{01}$ ,  $m_{11}$  and breakpoints  $\pm B_{P1}$ .

$N_{R_2}$  includes resistances  $R_4$ ,  $R_5$  and  $R_6$ . It has slopes  $m_{02}$ ,  $m_{12}$  and breakpoints  $\pm B_{P2}$ .

We will assume  $R_1 = R_2$  and  $R_4 = R_5$ .

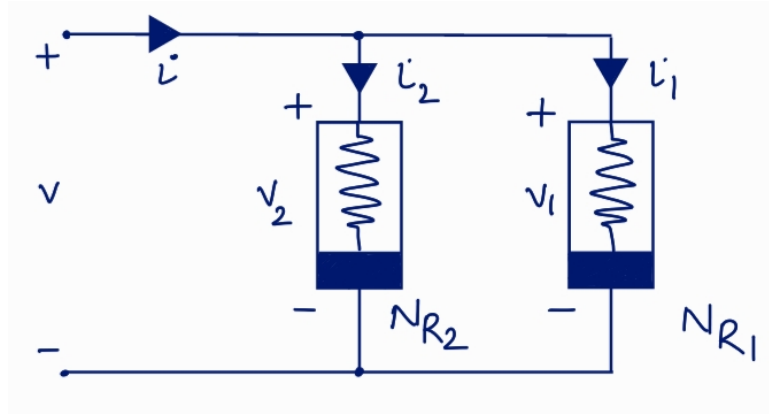


Fig 12. Non-linear Resistance

So for  $N_{R_1}$  we have :

$$m_{01} = \frac{1}{R_1} \quad ; \quad m_{11} = -\frac{1}{R_3} \quad ; \quad B_{P1} = \pm \frac{R_3}{R_2 + R_3} E_{sat} \quad (28)$$

For  $N_{R_2}$  we have :

$$m_{02} = \frac{1}{R_4} \quad ; \quad m_{12} = -\frac{1}{R_6} \quad ; \quad B_{P2} = \pm \frac{R_6}{R_5 + R_6} E_{sat} \quad (29)$$

Slopes of  $N_{R_1}$  and  $N_{R_2}$  are connected to the slopes of the combined graph is :

$$m_{11} + m_{02} = m_0 \quad ; \quad m_{11} + m_{12} = m_1 \quad (30)$$

The expected I-V graph of non-linear resistance is as follows :

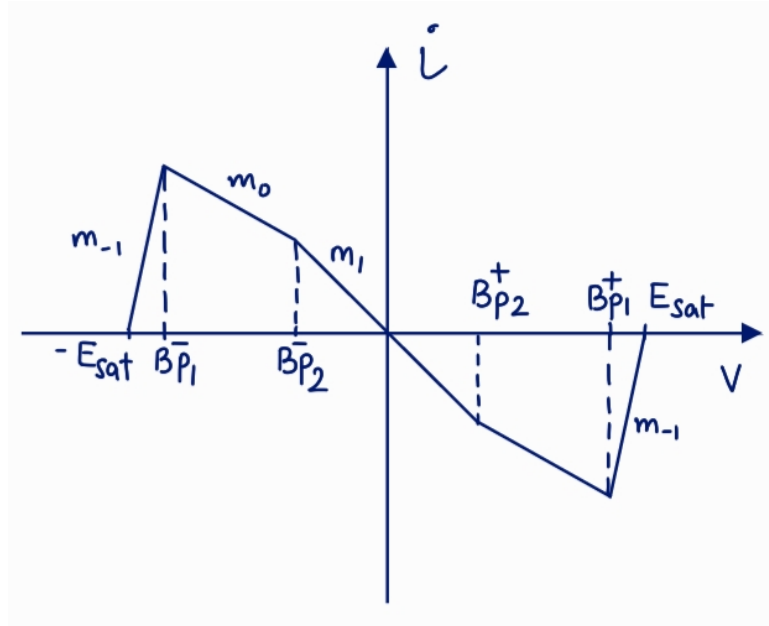


Fig 13. Expected I-V Characteristics of non-linear resistance

# V. Practical Implementation with LT-Spice

LTSpice was used to practically implement the Chua Circuit. The circuit design is used from the paper by Kennedy[put ref] (Fig 101).

All op-amps used are TL082, which was downloaded as a third-party tool from the website <http://www.chaotic-circuits.com/simulating-electronic-circuits/> and implemented into the circuit.

## 5.1 Setting Component Values

9V voltage sources were used to power the op-amps. The values of resistances, capacitors and inductors used to implement the circuit is as follows :

For  $N_{R_1}$  :

$$R_1 = 220\Omega \pm 5\%$$

$$R_2 = 220\Omega \pm 5\%$$

$$R_3 = 2.2k\Omega \pm 5\%$$

For  $N_{R_2}$  :

$$R_4 = 22k\Omega \pm 5\%$$

$$R_5 = 22k\Omega \pm 5\%$$

$$R_6 = 3.3k\Omega \pm 5\%$$

Rest of the circuit elements :

$$C_1 = 10nF \pm 5\%$$

$$C_2 = 100nF \pm 5\%$$

$$L = 18mH \pm 10\%$$

$$R = 2.0k\Omega \text{ to } 1.2k\Omega$$

$R$  is varied from  $2.0k\Omega$  to  $1.2k\Omega$  to observe the various stages of the bifurcation sequence.



## 5.2 Negative Resistances

First the negative resistances are individually implemented in LTSpice to ensure they function as we theoretically expect them to. The saturation voltage ( $E_{sat}$ ) for TL082 and breakpoints for both resistors is also obtained.

To measure the output voltage, a small resistance of value  $R = 10\Omega$  is put in series and the current across is plotted vs the input voltage.

### 5.2.1 $N_{R1}$

The values of slopes for  $N_{R_1}$  are obtained from (28) as :

$$\begin{aligned}m_{01} &= 4.545 \times 10^{-3}S = 4.545mS \\m_{11} &= -4.545 \times 10^{-4}S = -0.4545mS\end{aligned}$$

The values of sloped for  $N_{R_2}$  are obtained from (29) as :

$$\begin{aligned}m_{02} &= 4.545 \times 10^{-5}S = 0.04545mS \\m_{12} &= -0.303 \times 10^{-3}S = -0.303mS\end{aligned}$$

So the value of sloped for the